

VHDL Intermediate

Tarek Eldeeb, Valeo Expert

Prerequisites


Knowledge

- Basic VHDL Syntax knowledge
- Basic FPGA Technology knowledge
 - [Udemy Training](#)

Installed Tools

- Xilinx tools (ISE/XPS 14.7) should be preinstalled with debugger drivers.
- Xilinx development kit with Spartan FPGA
 - [ISE/XPS Download](#)

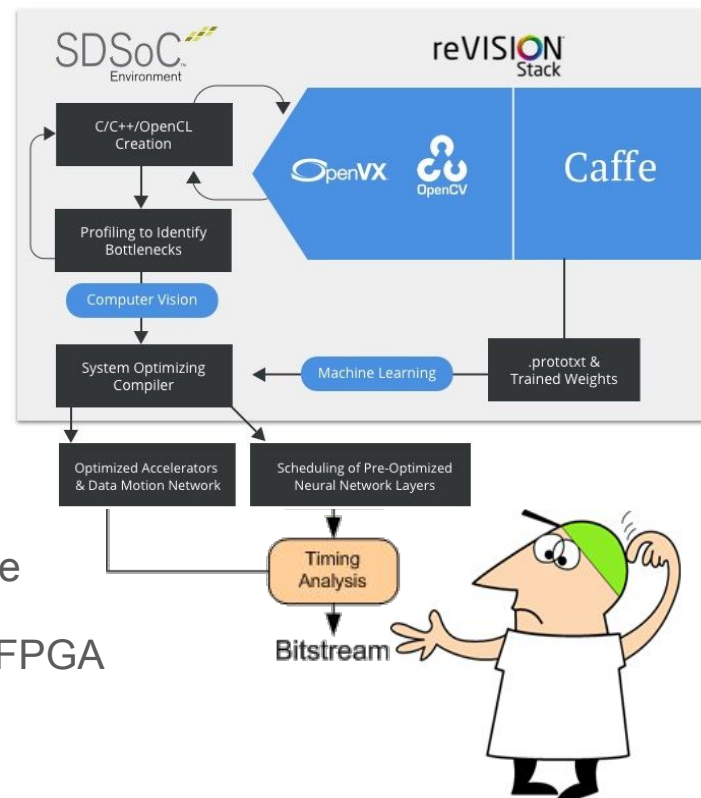SDSoc: [Xilinx Tutorials](#) - [Demo Video](#)



Training Outline

Day #1


- Revision: VHDL I
- Pipelining
- Static Timing Analysis
- Exercise

Day #2

- FPGA Advanced:
 - IO banks and Clocks
 - Special blocks
- AXI Bus: Specs and Applications
- Exercise

Day #3: Practical Workshop

- Analyse Current Design
- Redesign for expandability

 

April 2020 | VHDL II

Valeo

Revision

Rule #1: We are describing a HW circuit!


When you are describing hardware in VHDL, you are only describing the behaviour. The actual circuit will be synthesized (by the tools, eg. Xilinx ISE) to gates. The FPGA then implements the gates. The FPGA does NOT execute the VHDL code directly!!



April 2020 | VHDL II

Valeo

Revision

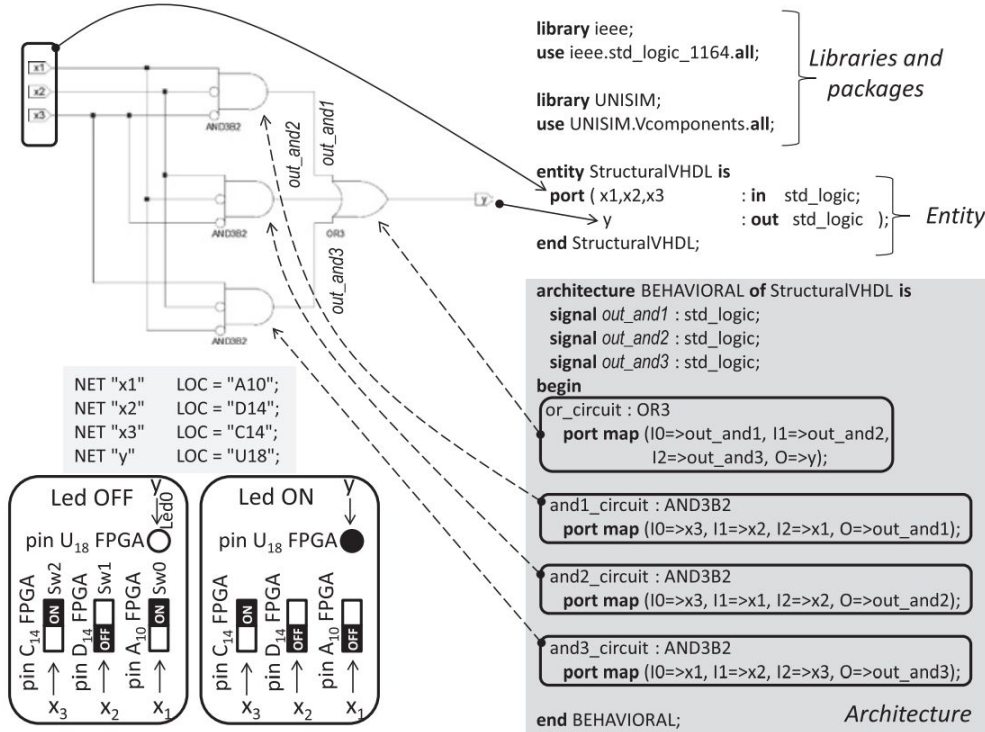

April 2020 | VHDL II



Revision

Declaration of libraries:

```

library . . . ;
use . . . ;
. . . . .
    
```

Description of entity

```

entity <name of entity> is
    Declaration of generic parameters
    Declaration of ports
end <name of entity>;
    
```

Description of architecture

```

architecture <name of architecture> of <name of entity> is
    Declaration of signals
    Declaration of constants
    Declaration of types
    Declaration of components
    Declaration of functions (with bodies)
    Declaration of procedures (with bodies)
    Declaration of shared variables
begin
    Body of architecture
end <name of architecture>;
    
```

Connected components which are either library primitives or previously designed circuits from:

- HDL specifications
- schematic specifications
- IP cores

Structural

Mixed

Behavioral

Examine VHDL code and component instantiation for schematic entries


Concurrent constructions:

- signal assignments
- VHDL processes

Xilinx ISE Design tab

Design Utilities

View HDL Functional Model
View HDL Instantiation Template

 

April 2020 | VHDL II



Revision

1 **library** IEEE;
use IEEE.std_logic_1164.all; } use of libraries and packages


Interface

2 **entity** half_adder **is**
port (A : **in** STD_LOGIC;
B : **in** STD_LOGIC;
carry_out : **out** STD_LOGIC;
sum : **out** STD_LOGIC);
end half_adder;

Architecture

3 **architecture** half_adder_behavior **of** half_adder **is**
begin
sum <= A **xor** B;
carry_out <= A **and** B;
end half_adder_behavior;

HA

 

A	B	carry_out	sum
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

April 2020 | VHDL II

Revision


```
library IEEE;
use IEEE.std_logic_1164.all;
entity FULLADD is
port ( A, B, carry_in : in std_logic;
      sum, carry_out : out std_logic );
end FULLADD;
architecture STRUCT of FULLADD is
signal s1, s2, s3 : std_logic;
begin
  u1: entity work.half_adder
      port map(A, B, s2, s1);
  u2: entity work.half_adder
      port map(s1, carry_in, s3, sum);
  carry_out <= s2 or s3;
end STRUCT;
```

Example of positional association

```
library IEEE;
use IEEE.std_logic_1164.all;
entity half_adder is
port (
  A : in STD_LOGIC;
  B : in STD_LOGIC;
  carry_out : out STD_LOGIC;
  sum : out STD_LOGIC );
end half_adder;
architecture half_adder_behavior of half_adder is
begin
  sum <= A xor B;
  carry_out <= A and B;
end half_adder_behavior;
```

A	B	carry_in	carry_out	sum
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

FULLADD

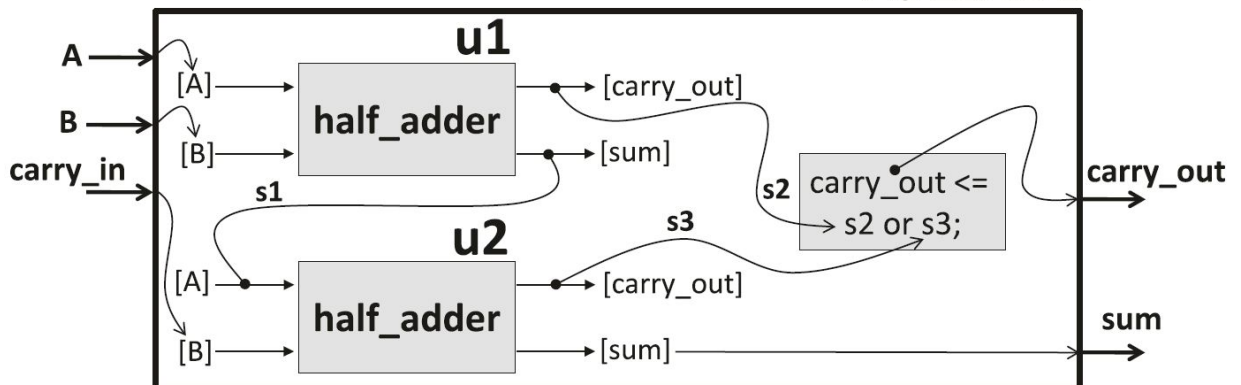


April 2020 | VHDL II

TIPs: Packages/Types

```
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_textio.all;
use IEEE.std_logic_arith.all;
use IEEE.numeric_bit.all;
use IEEE.numeric_std.all;
use IEEE.std_logic_signed.all;
use IEEE.std_logic_unsigned.all;
use IEEE.math_real.all;
use IEEE.math_complex.all;
```

What to use?

```
library ieee;
use ieee.std_logic_1164.all; -- UX01ZWLH
use ieee.numeric_std.all; -- un/signed
use ieee.std_logic_arith.all; -- bad, old!
```

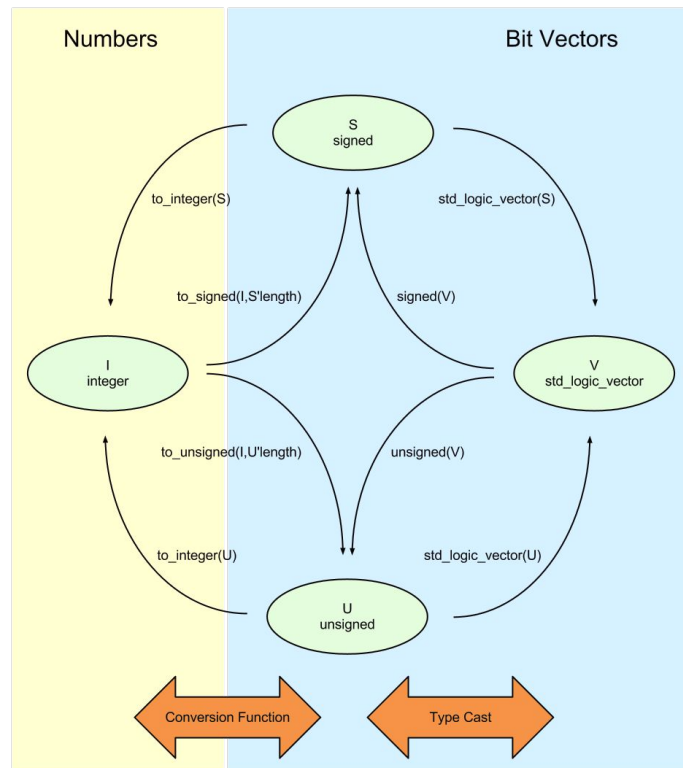

April 2020 | VHDL II



TIPs: Attributes

This code is NOT accepted: VHDL is hard-typed

```
b(0 to 7) <= a(7 downto 0)
```

- signal'event
- signal'left/right
- signal'low/high
- signal'length
- signal'range
- signal'reverse_range



```
Sol#1
function reverse_any_vector (a: in std_logic_vector)
return std_logic_vector is
    variable result: std_logic_vector(a'RANGE);
    alias aa: std_logic_vector(a'REVERSE_RANGE) is a;
begin
    for i in aa'RANGE loop
        result(i) := aa(i);
    end loop;
    return result;
end; -- function reverse_any_vector
```

```
Sol#2
signal a : std_logic_vector(0 to 7);
signal b : std_logic_vector(7 downto 0);
..
for i in a'range generate
    b(i) <= a(i)
end generate;
```

April 2020 | VHDL II



TIPs: Process

Processes should be broken till each has a **SINGLE** type:

1. Pure Combinational
2. Pure Sequential
3. Sequential with async reset



April 2020 | VHDL II

Valeo

TIPs: Process

1- Pure Combinational

- Rule 1: Every input (that can affect the output(s)) must be in the sensitivity list.
- Rule 2: Every output must be assigned a value for every possible combination of the inputs

```
process (A, B)
begin
  if (SEL = '0') then
    Y <= A;
  else
    Y <= B;
  end if;
end process;
```

```
process (SEL, A, B)
begin
  if (SEL = '0') then
    Y <= A;
  end if;
end process;
```

April 2020 | VHDL II

Valeo


TIPs: Process

2- Pure Sequential

- Rule 1: Only the clock should be in the sensitivity list
- Rule 2: Only signals that change on the same edge of the same clock should be part of the same process

```
process (CLK)
begin
  if (CLK'event and CLK='1') then
    Z <= A and B;
  end if;
end process;
```

rising_edge(clk) →

 


April 2020 | VHDL II

TIPs: Process

3- Sequential with async reset

```
process (CLK, RESET)
begin
  if (RESET = '1') then
    Z <= '0';
  elsif (CLK'event and CLK='1') then
    Z <= A and B;
  end if;
end process;
```

 

April 2020 | VHDL II

Quiz Time :-)

```

entity TestCombProc is
port ( clk : in std_logic;
      BTND : in std_logic;
      led : out std_logic_vector(1 downto 0) := (others=> '0') );
end TestCombProc;
architecture Behavioral of TestCombProc is
    Signal B : std_logic := '1';
    Signal A : std_logic := '0';
begin
    test_assign: process(clk)
    begin
        if rising_edge(clk) then
            if BTND = '1' then led <= A & B;
            else
                if B = '1' then
                    A <= B;
                    B <= A;
                    led(1) <= A;
                    led(0) <= B;
                end if;
            end if;
        end if;
    end process test_assign;
end Behavioral;


```



April 2020 | VHDL II



Quiz : Answered

 

April 2020 | VHDL II

