
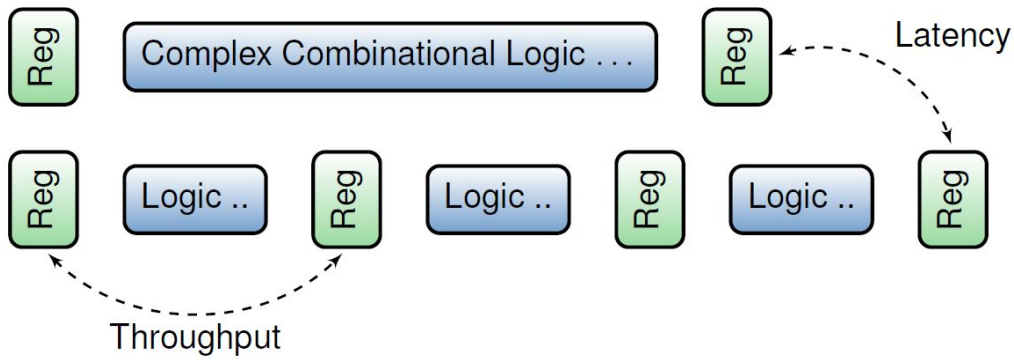


Pipelines

 


- Area?
- Power?
- Optimal number of stages?
- Automatic Register Balancing



April 2020 | VHDL II

Pipelines

- Does **Feedback** break the pipe?

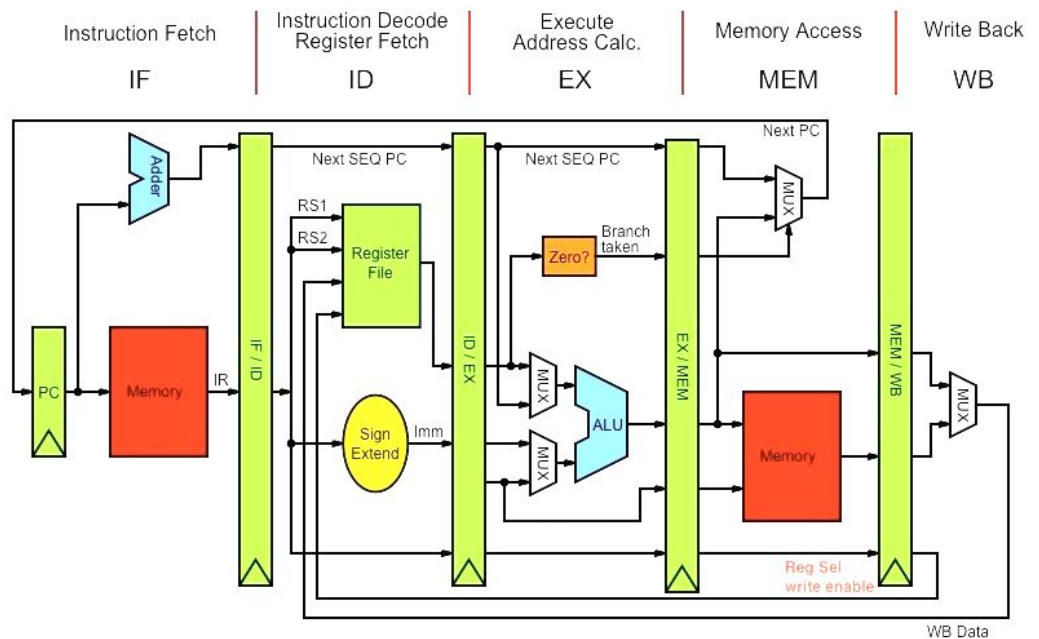

WB Data




April 2020 | VHDL II



Lab #1


1. Write a vhdl module that adds 4 x 18bit registered inputs, and deliver the result at the clock positive edge
2. Write a TB to check results
3. Analyse
 - a. RTL Schematics
 - b. Technology Schematics
 - c. Post PAR static timing
4. Add pipeline stages, calculate on 2 steps
5. Do steps 2~3
6. ~~Add 3 shift registers at output~~
7. ~~Do steps 2~3~~
8. ~~Enable register balancing~~
9. ~~Do steps 2~3~~

Pipelines

   


- CPU: Who breaks the pipeline?
- What sets the limits to other digital designs?

Pipelines: Latches


 


INPUT		OUTPUT
A	B	A NAND B
0	0	1
0	1	1
1	0	1
1	1	0

 

SR latch operation		
S	R	Action
0	0	not allowed
0	1	Q = 1
1	0	Q = 0
1	1	No Change

[anim](#)

  




- Latch:
- IO Ports
 - Incomplete statements!

- MS Edge D-Flip Flop:
- Registers
 - Negative edge?

Why latches have poor timing?

April 2020 | VHDL II

Pipelines: Latches

   

April 2020 | VHDL II


Pipelines: Latches

- Setup Time
- Hold time
- Clock-to-Output time

Maximum Combinational Delay



$$\frac{T_{clk} - T_{co} - T_{su}}{1/F_{max}}$$

 - Metastability:
 - Respect T_{su} and T_h
 - Practical range?
 - System inputs?
- In a shift register, Can $T_{co} < T_h$?




Pipelines: Out-of-the-box!

- Multi-valued Logic
- Wave pipelining!

  

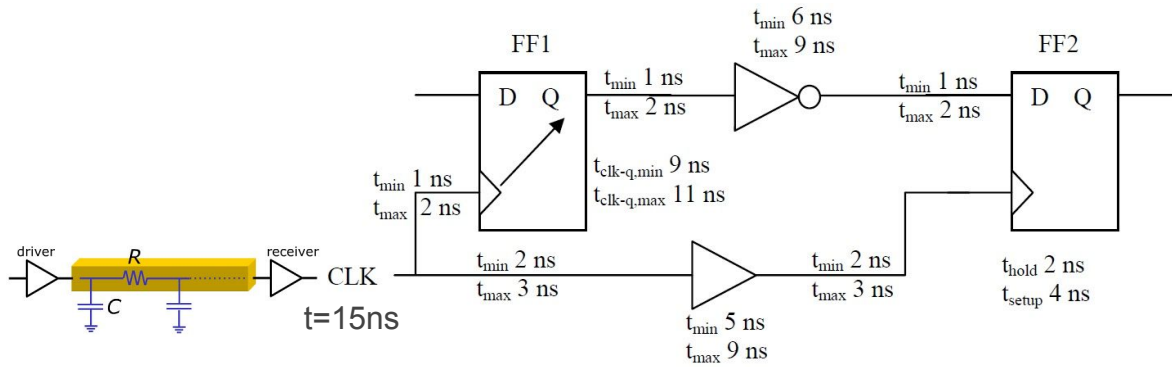Static Timing Analysis: Setup/Hold Violation?



Hold Analysis: Will new data overwrite the old at FF2?


- Min Data Delay
- Max Clock Delay
- $T_{clk-Td} = 18-17 = +ve \text{ slack}$

Setup Analysis: Will data miss the sampling edge at FF2?

- Max Data Delay
- Min Clock Delay
- $T_{clk-Td} = 20-26 = -ve \text{ slack}$


Static Timing Analysis

 1. Reg-to-Reg delay [16ns]
 - a. Possibilities?
2. Input Setup time [12-2ns]
 - a. $T_{su} + \text{Max.Td} - \text{Min.Tck}$
3. Input Hold time [-2ns]
 - a. $T_{hd} + (\text{Max.Tck} - \text{MinTd})$
4. Clock-to-Output delay [22ns]
 - a. Critical path?
5. Pin-to-Pin Combinational delay [16ns]
6. Max Clock frequency?
 - a. $1/\text{Max}(\text{Reg2Reg}, \text{Clk2Out}, \text{Pin2Pin})$



Register IOs?

Static Timing Analysis

 

- Multiple Paths => Min, Max
- Backtrace method
- Combinational loops?
- System: Where to optimize?

